



$$a) \Delta V_{DA} = |2(I_2 - I_1)| + |12(I_3 - I_2)| = 8,54V$$

$$\Delta V_{FC} = 30V - 10I_2 = 20,38V$$

$$M_1: 0 = -6V + 2(I_2 - I_1) + 6(I_3 - I_1) - 3I_1$$

$$M_2: 0 = 6(I_1 - I_3) + 12(I_2 - I_3) + 12V$$

$$M_3: 0 = -24V - 10I_2 - 6I_2 + 12(I_3 - I_2) + 2(I_1 - I_2)$$

$$6 = -11I_1 + 2I_2 + 6I_3$$

$$-12 = 6I_1 - 18I_3 + 12I_2$$

$$24 = -30I_2 + 2I_1 + 12I_3$$

$$\Delta S = \begin{vmatrix} -11 & 2 & 6 \\ 6 & 12 & -18 \\ 2 & -30 & 12 \end{vmatrix} = 2916$$

$$I_1 = \frac{\begin{vmatrix} 6 & 2 & 6 \\ -12 & 12 & -18 \\ 24 & -30 & 12 \end{vmatrix}}{2916} = -\frac{2520}{2916} = -864 \text{ mA} \checkmark$$

$$I_2 = \frac{\begin{vmatrix} -11 & 6 & 6 \\ 6 & -12 & -18 \\ 2 & 24 & 12 \end{vmatrix}}{2916} = -\frac{2808}{2916} = -962 \text{ mA} \checkmark$$

$$I_3 = \frac{\begin{vmatrix} -11 & 2 & 6 \\ 6 & 12 & -12 \\ 2 & -30 & 24 \end{vmatrix}}{2916} = -\frac{768}{2916} = -263 \text{ mA} \checkmark$$

1 AN

NEGATIVAS

POQUE ME

EQUIVOQUE  
EL SENTIDO

b)

$$P_{BAT} = 24I_2 + 6I_1 - 12I_3 = 25,116 \text{ W}$$

$$P_{3\Omega} = 3I_1^2 = 2,23 \text{ W}$$

$$P_{6\Omega} = 6I_2^2 = 5,55 \text{ W} \checkmark$$

$$P_{6\Omega I_1} = 6(I_3 - I_1)^2 = 2,76 \text{ W} \quad P_{10\Omega} = 10I_2^2 = 9,254 \text{ W}$$

$$P_{2\Omega} = 2(I_2 - I_1)^2 = 0,079 \text{ W}$$

$$P_{12\Omega} = 12(I_3 - I_2)^2 = 5,863 \text{ W}$$

$$c) Q = P \cdot t$$

$$Q = 0,079 \cdot 1800$$

$$Q = 341,2 \text{ J}$$